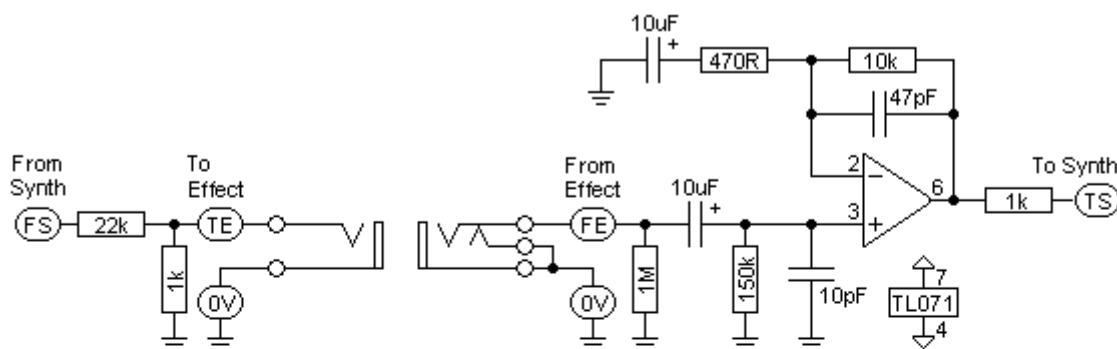


Stomp Box Adapter


The previous version can be found [here](#).

This is a new version of the Stomp Box Adapter. This time there is no provision for any jacks on the PCB. It can be used as an external input amplifier, a way to use effects pedals with synthesizer signal levels, or a way to use synthesizer modules with instruments such as electric guitars.

A little on how it works:



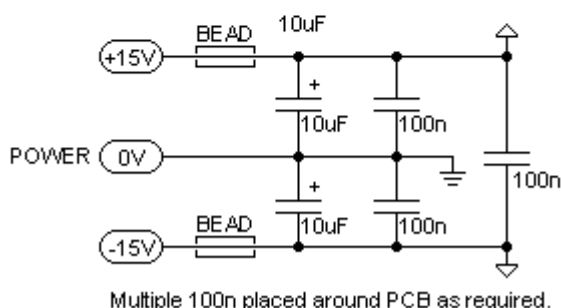Schematic for one of three identical modules.



CGS60 VER2.0 External Input Module (Stomp Box Adapter)

Copyright 2010 by Ken Stone


R = ohms

The schematic of the Stomp Box Adapter. The jacks shown on the diagram are for connection to the stomp-box. Note that the switching contact on the input jack is connected to 0V.


Modular synthesizers generally use much higher signal levels than are used in effects pedals, so directly connection the two will create two problems. First, the excessive signal will cause the input of the effects pedal to overload/distort. Second, the output from effects pedal is too weak to drive synthesizer modules without some amplification. To compensate for these problems, the signal from the synthesizer must be dropped to a fraction of what it was, while the output of the effects pedal must be amplified by the same amount to restore it to a level suitable for the synthesizer. I have chosen to use a ratio of 20 as this encompasses the signal levels of many synths. If you know for certain that the ratio is too great, the ratio can be reduced to reduce the amplification of any effects pedal noise. For example, if an effects pedal works on a 1V p-p signal, and a synthesizer has a maximum output of 5V p-p, a ratio of 5 would be adequate.

The preamplifier of the stomp box adapter is a basic non-inverting amplifier with an AC gain of 20, and suppression capacitors as needed. The input impedance is approximately 150k. The AC gain can be reduced if need by by increasing the value of the 470R resistor. For


Construction

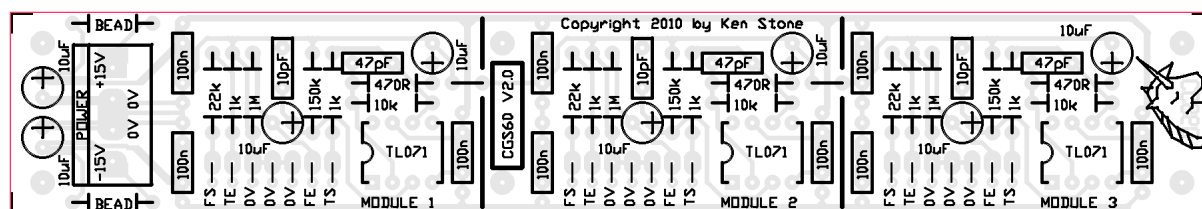

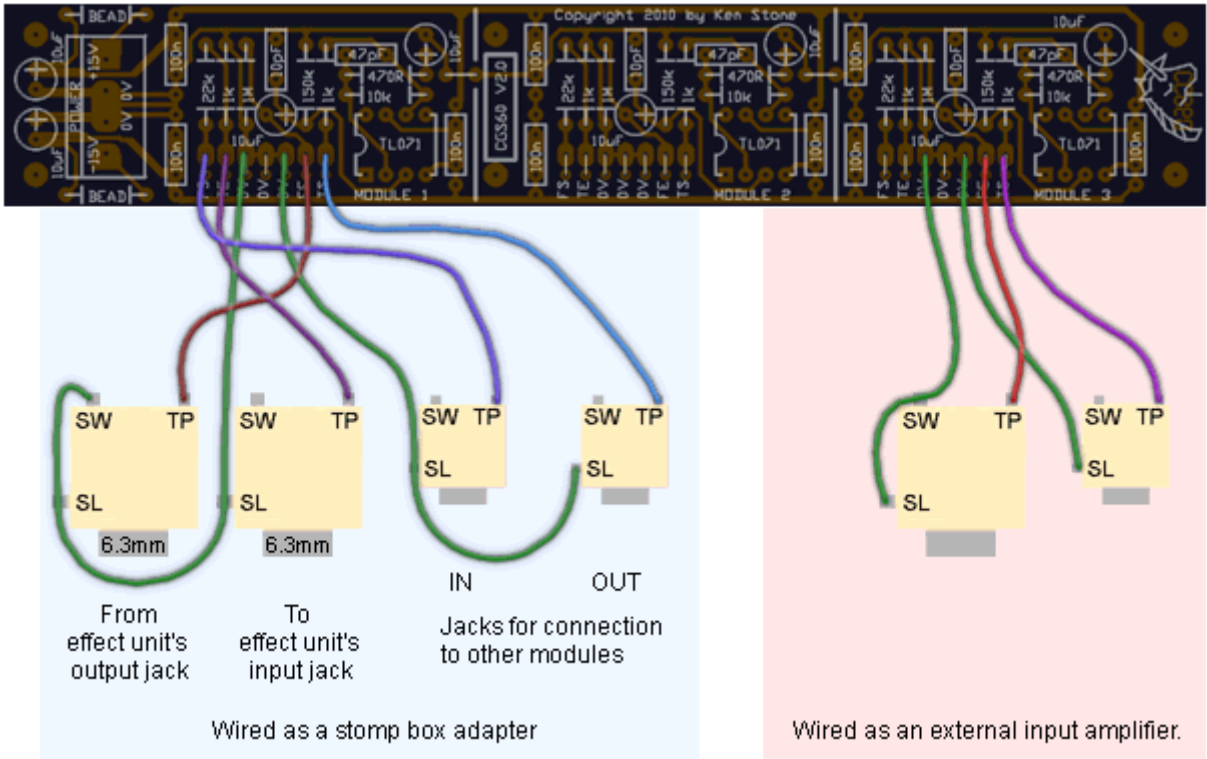- 1) Trim off the end of a suitable gauge of hookup wire
- 2) Pass it through the larger (pad-less) hole from below and pull a couple of inches through.
- 3) Strip the insulation from the end of the wire, twist and tin it.
- 4) Bend the wire over and pass the tinned part through the associated pad hole. Trim as needed.
- 5) Flip the board and solder the tinned wire to the pad.
- 6) Pull the excess wire back through the first hole so only a short length remains between the hole and the second pad. Make sure this is the LAST step, or the insulation will peel back from the wire as it is soldered.



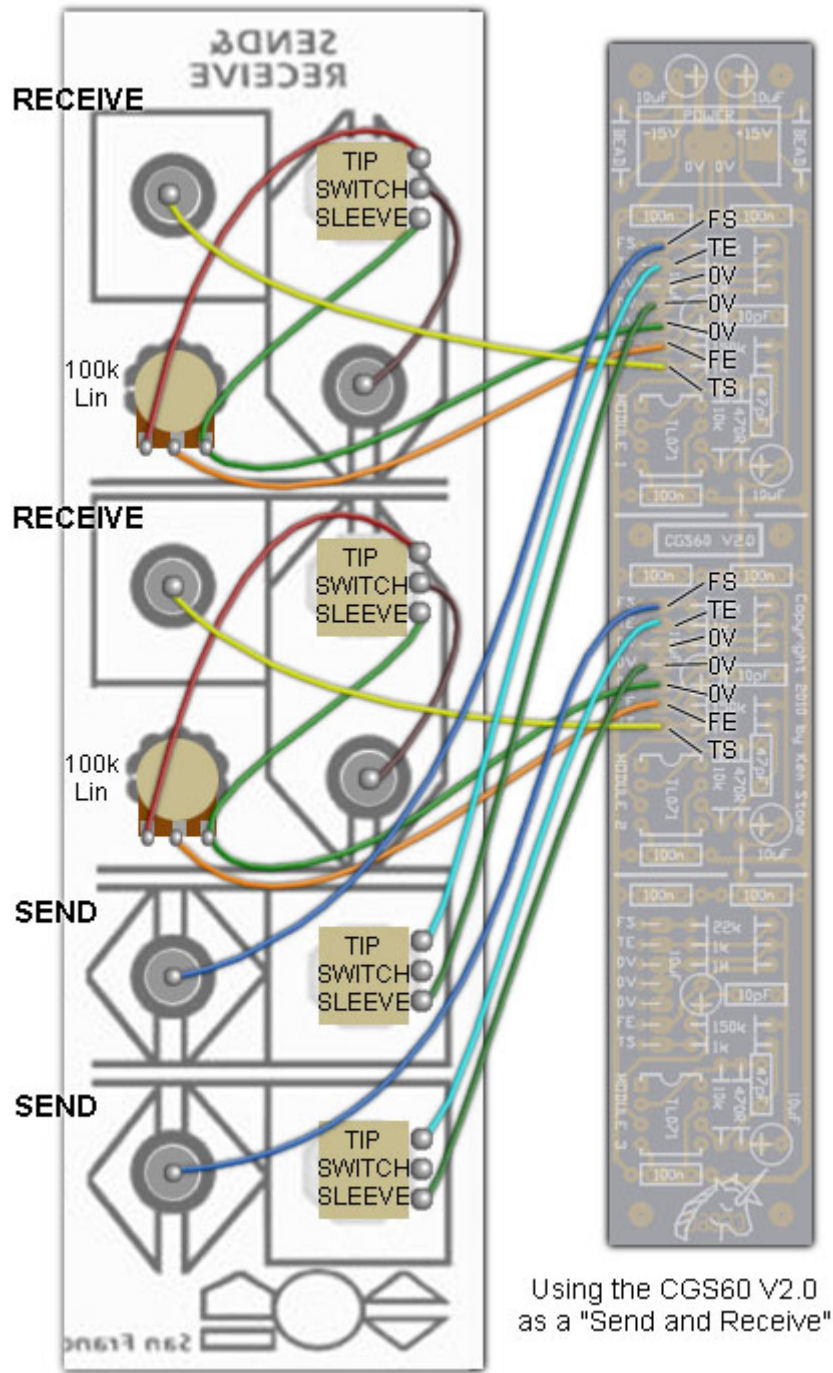Two examples of how this board can be wired.



How to wire the CGS60 V2.0 as a Send and Receive module.

Notes:

- The module will run on +/-12 volts or +/- 15 volts with no changes.
- **PCB info:** 6" x 1" with 3mm mounting holes 0.15" in from the edges.
- Please [email me](#) if you find any errors.

Parts list

This is a guide only. Parts needed will vary with individual constructor's needs.

If anyone is interested in buying these boards, please check the [PCBs for Sale](#) page to see if I have any in stock.

Can't find the parts? See the [parts FAQ](#) to see if I've already answered the question. Also see the

Part	Quantity
Capacitors	
10pF	3
47pF	3
100n	9
10uF 25V	8
Resistors	
470R	3
1k	6

[CGS Synth discussion group.](#)

10k	3
22k	3
150k	3
1M	3
Semi's	
TL071	3
Misc.	
Ferrite Bead (or 10R resistor)	2
0.156 4 pin connector	1
CGS60 VER2.0 PCB	1

Article, art & design copyright 2010 by [Ken Stone](#)

[Modular Synth Home](#)

[Disclaimer](#)